

Volts

I can observe and explain the effects of differing volts in a circuit.



	0V	1.5V	3.0V	4.5V
Prediction				
Results				
	0V	1.5V	3.0V	4.5V
Prediction				
Results				
	0V	1.5V	3.0V	4.5V
Prediction				
Results				