
*


Interpreting and Drawing Circuit Diagrams


I can recognise and draw scientific circuit symbols.

Use the Scientific Circuit Symbols Mat to help.

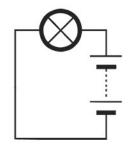Look at the circuits below and label each part.



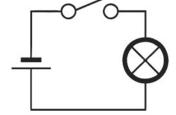

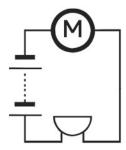

Draw the following circuit using the scientific circuit symbols.

